

1.

a. Define half adder.

A half adder is a type of adder, an electronic circuit that performs the addition of numbers. The half adder can add two single binary digits and provide the output plus a carry value.

b. Draw a truth table for the sum and carry of half adder.


INPUT A	INPUT B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

c. Write the sop expression from the truth table.

Sum of product =  $A'B + AB'$

Carry of product =  $A.B$

d. Draw the circuit using logsim.

 

2. a. Draw the truth table for the outputs of the full adder.

INPUT A	INPUT B	CARRY IN	SUM	CARRY OUT
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

b. Write the corresponding sop expression for sum and carry of full adder and simplify the expression


$$(A.B.C') + (A.B'.C) + (A'.B.C) + (A.B.C)$$

$$\begin{aligned}
 &= (A.B.C') + (A'.B.C) + (A.B.C) + (A'.B'.C) \\
 &= C'(A.B + A'.B) + C(A.B + A'.B) \\
 &= C'(A \oplus B) + C(A \oplus B) \\
 &\text{Let } A \oplus B \text{ be } x \\
 &= C'x + Cx \\
 &= C \oplus x \\
 &\text{Substituting value of } x, \\
 &= C \oplus (A \oplus B) \\
 &= C \oplus A \oplus B
 \end{aligned}$$

$$(A.B.C)+A.B'C)+(A'B.C)+(A.B.C)$$

$$\begin{aligned}
 &= A B \bar{C} + A \bar{B} C + \bar{A} B C + A B C \\
 &= A B \bar{C} + A B C + A \bar{B} C + A B C + A B C \\
 &= A B \bar{C} + A B C + A \bar{B} C + \bar{A} B C + A B C \\
 &= A B (\bar{C} + C) + B C (\bar{A} + A) + A \bar{B} C \\
 &= A B + B C + A \bar{B} C \\
 &= A B + C (B + A \bar{B}) \\
 &= A B + C (B + A) \quad \{ (B + A) (B + \bar{B}) \} \\
 &= A B + C (B + A) \\
 &= A B + C (B + A) \\
 &= A B + B C + A C
 \end{aligned}$$

 c. Draw full adder using two half adder and an OR gate.




prepared by ABHISHEK


3. Using the three stages of design, construct the circuits for the following input /output values. Here A, B and C are the inputs whereas D, E, F, G, H and I are outputs. Note: Draw circuit diagram using logsim corresponding to the simplified expression of outputs D, E, F, G, H and I.

A	B	C	D	E	F	G	H	I
0	0	0	1	0	1	0	1	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	1	1	1
1	0	0	1	0	0	1	0	1
1	1	1	1	1	1	1	1	1
1	1	0	1	1	0	1	0	1
1	0	1	1	1	1	1	1	0
0	1	1	0	0	0	1	1	1


Output: D

 


Output: E

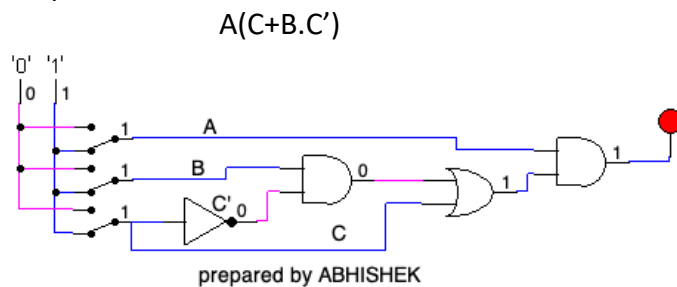


OUTPUT: F

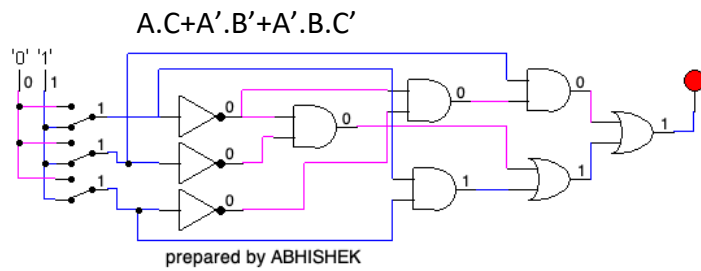

Output: G

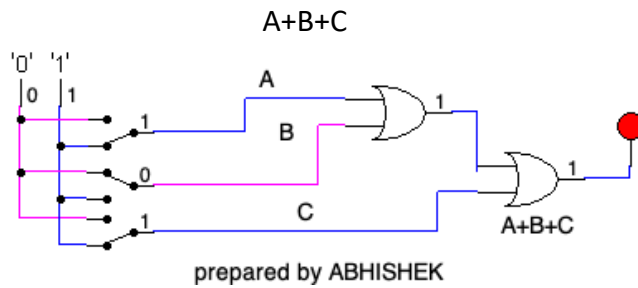

Output: H

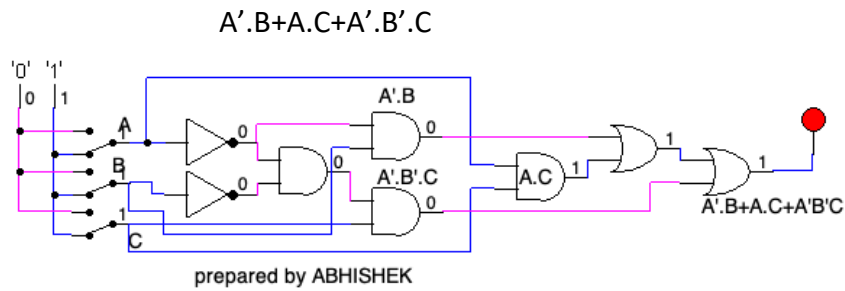

Output: I

