

Instruction:

Complete all questions in **2 hour**.

Group: A

1. Unit of computer capable of performing arithmetic, logical and data manipulation operation on binary numbers is called
 - CU
 - ✓ ALU
 - I/O units
 - Processing Unit

2. Arithmetic logic unit
 - ✓ perform arithmetic operations
 - store data
 - perform comparison
 - communicate with input devices
 - From above Correct one is.
 - I only
 - II only
 - I and II only
 - ✓ I and III only

3. Which of the following is component of ALU?
 - Functional Unit
 - Multiplexor
 - Instruction Decoder
 - ✓ All of the Above

4. Operations of Computer Arithmetic and logic unit is directed by
 - ALU itself
 - Program
 - ✓ Control Unit
 - Memory Unit

5. An arithmetic logic unit (ALU) is a _____ digital electronic circuit.
 - ✓ Combinational
 - Sequential
 - Both
 - None of above

6. Engineering design of arithmetic logic unit determines the
Type and number of storing operations
Type and number of logical operations
Type and number of control operations
✓ Type and number of logical and arithmetic operations
7. Which is the function of Decoder?
Perform logic and arithmetic operation
✓ Selects the output we want from ALU
Send output choice made through the decoder
None of the above
8. Which of the following is the function of Multiplexor?
Perform logic and arithmetic operation
Selects the output we want from ALU
✓ Send output choice made through the decoder
None of the above
9. Both addition and subtraction can be performed by a single circuit using _____
Multiplexor
✓ Controlled Inversion
Half Adder
Fuller Adder

Group B


10. Design a combinational Logic circuit that selects and generates any of the following logic and arithmetic functions listed below.

A XOR B

A NOR B


A + B

A - B

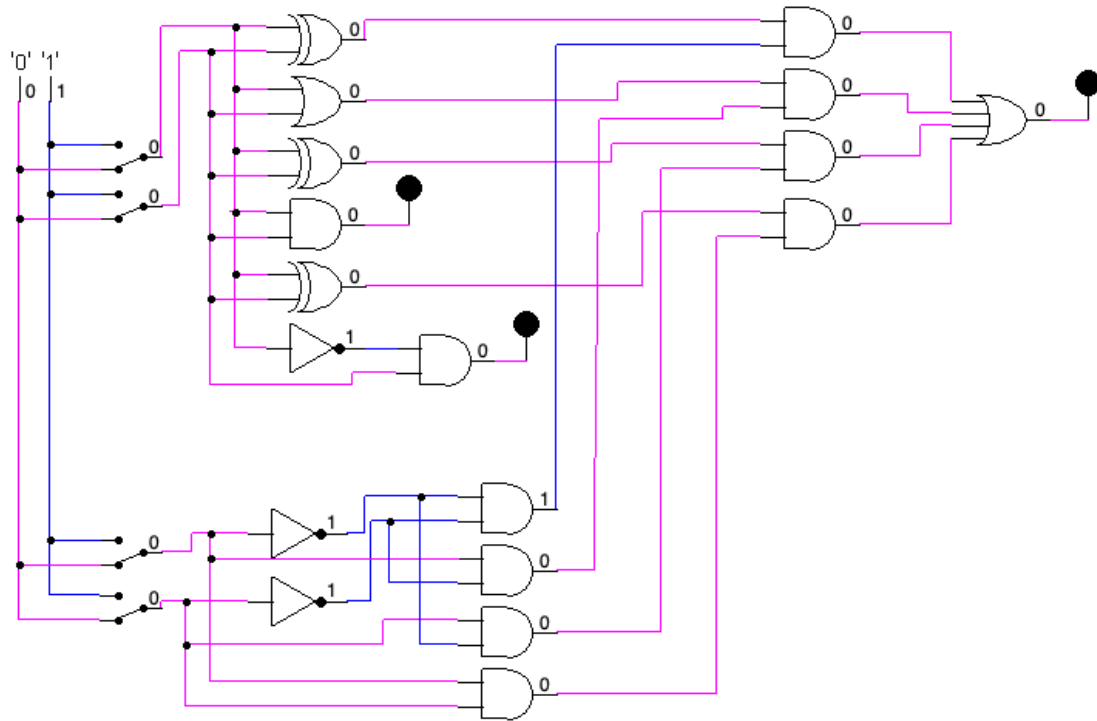

design by abhishek

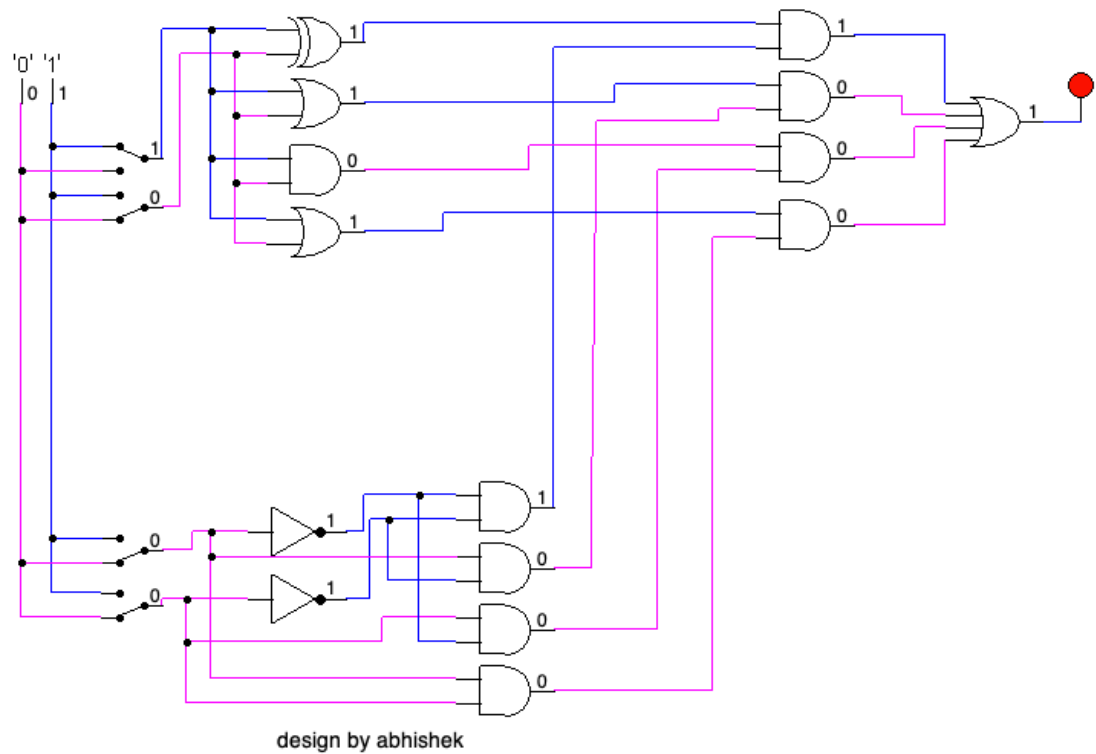11. Design a digital circuit that performs the four logical operations of exclusive-OR, NOR, NAND and OR. Use two selection variables. Show the logic diagram of one typical stage. Discuss the working mechanism of the circuit that you have constructed.



12. Following diagram shows a 4-bit adder/subtractor. Design the circuit diagram using Logsim. Discuss how the circuit performs addition and subtraction.

